

## LAB # 8

Name: \_\_\_\_\_

Reg#: \_\_\_\_\_

### **Aim:**

To get better understanding of time shared architecture and working of state machines with FPGA Spartan6 Boards.


### **Introduction:**

#### State Machine:

State Machine is a flowchart like graphical notation that describes the cycle by cycle operations of an algorithm and its each step takes one clock cycle. It describes behavior rather than structure and provides a mechanism for performing systematic step-by-step design step design. They can be directly translated to Verilog code and used to design synchronous sequential circuits.
 
#### Example:

Generating 1 at the output after counting four number of 1's on a serial interface.



### **Tasks:**

- TASK 1:**

Using Spartan6 FPGA board identify the pattern  $(1101)_{\text{series}}$  and once pattern is identified turn the LED on.

- **TASK 2:**

**Design a time shared architecture using single multiplier and single adder of the following difference equation.**

**where  $f_{\text{sys}}/f_s = 4$ .**



$$Y[n] = b_0x[n] + b_1x[n-1] + b_2x[n-2] + a_1y[n-1]$$